

## Sequential Part Assignment

>Sadman Sakib

>2232058642

### Counter Using T Flip Flop

Counts :

0 to 6 (Since, in combinational part 111(7) is set for Don't care)

: 000-001-010-011-100-101-110-Repeat(000)

Current State			Next State			T Flip Flop Outputs		
$Q_C$	$Q_B$	$Q_A$	$Q_{CN}$	$Q_{BN}$	$Q_{AN}$	$T_A$	$T_B$	$T_C$
0	0	0	0	0	1	1	0	0
0	0	1	0	1	0	1	1	0
0	1	0	0	1	1	1	0	0
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	1	0	0
1	0	1	1	1	0	1	1	0
1	1	0	0	0	0	1	0	1

K-Maps :

$T_A$ :

$Q_C / Q_B \ Q_A$	00	01	11	10
0	1	1	1	1
1	1	1	x	1

Eqn: 1

$T_B$ :

$Q_C / Q_B \quad Q_A$	00	01	11	10
0	0	1	1	0
1	0	1	x	0


Eqn:  $Q_A$

$T_C$ :

$Q_C / Q_B \quad Q_A$	00	01	11	10
0	0	0	1	0
1	0	0	x	1

Eqn:  $Q_A \cdot Q_B + Q_C \cdot Q_B$

Circuit:

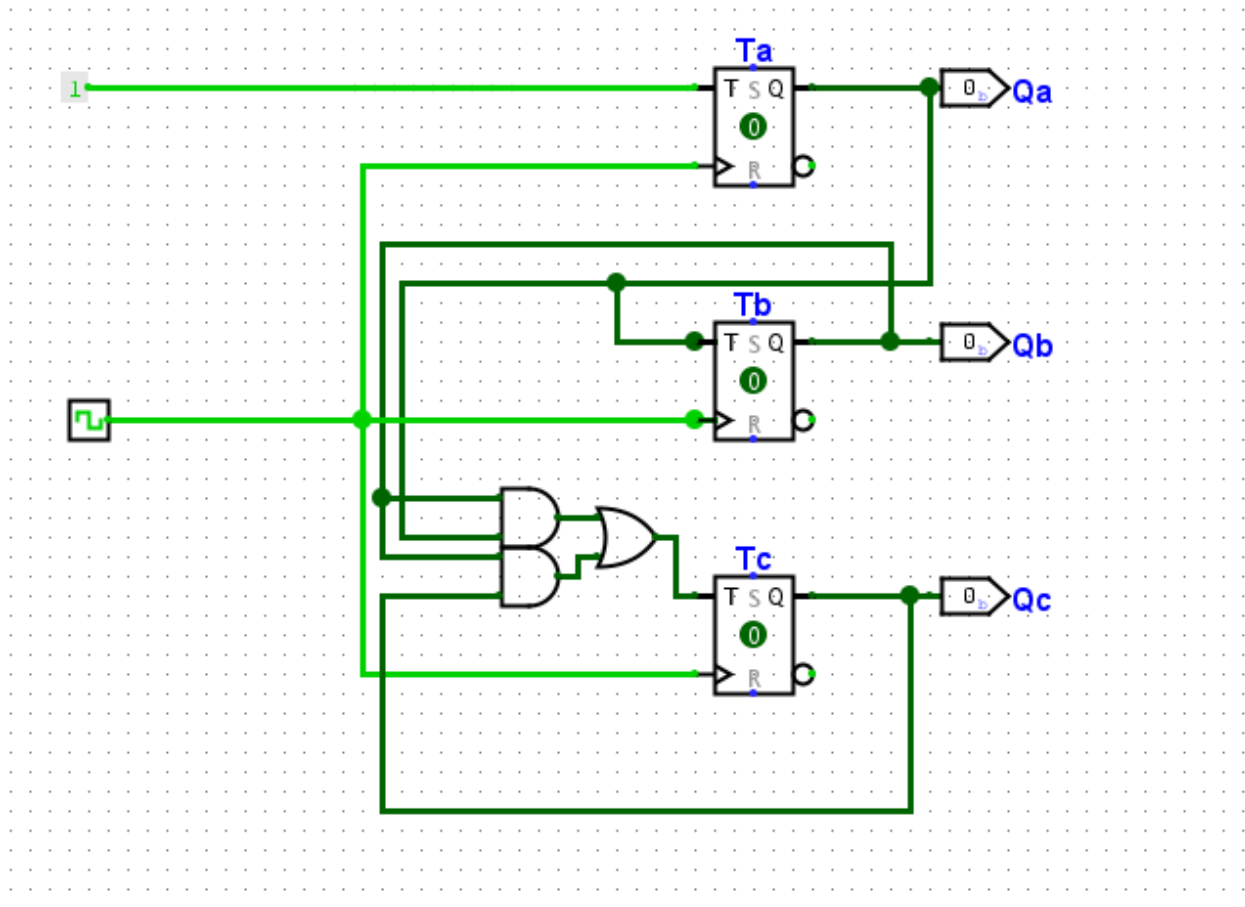

### Cost Analysis :

Since T flip flop isn't available in market

We can sort JK to T

2xJK Flip Flop IC 7476 :  $36 \times 2 = 72$  BDT

1x2 input OR IC : 7432 :  $30 \times 1 = 30$  BDT

1x2 input AND IC : 7408 :  $30 \times 1 = 30$  BDT

Total : 132 BDT

### Counter Using D Flip Flop

Counts :

0 to 6 (Since, in combinational part 111(7) is set for Don't care)

: 000-001-010-011-100-101-110-Repeat(000)

Current State			Next State			D Flip Flop Outputs		
$Q_C$	$Q_B$	$Q_A$	$Q_{CN}$	$Q_{BN}$	$Q_{AN}$	$D_A$	$D_B$	$D_C$
0	0	0	0	0	1	1	0	0
0	0	1	0	1	0	0	1	0
0	1	0	0	1	1	1	1	0
0	1	1	1	0	0	0	0	1
1	0	0	1	0	1	1	0	1
1	0	1	1	1	0	0	1	1
1	1	0	0	0	0	0	0	0

### K-Maps :

$D_A$ :

$Q_C / Q_B \ Q_A$	00	01	11	10
0	1	0	0	1
1	1	0	x	0

Eqn:  $Q_C' \cdot Q_A' + Q_B' \cdot Q_A'$

$D_B$ :

$Q_C / Q_B \ Q_A$	00	01	11	10
0	0	1	0	1
1	0	1	x	0


Eqn:  $Q_B' \cdot Q_A + Q_C' \cdot Q_B \cdot Q_A'$

$D_C$ :

$Q_C / Q_B \ Q_A$	00	01	11	10
0	0	0	1	0
1	1	1	x	0

Eqn:  $Q_B \cdot Q_A + Q_C \cdot Q_B'$

Circuit :

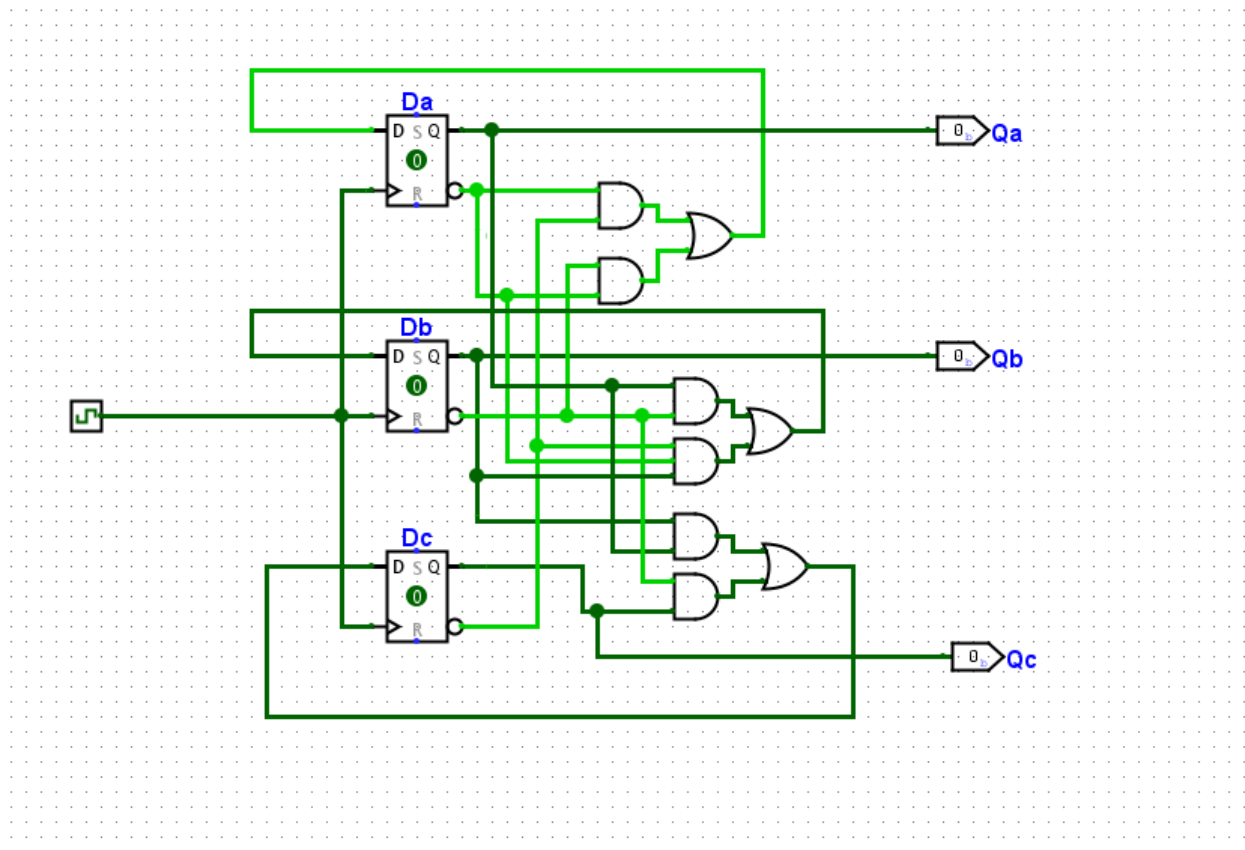

### Cost Analysis :

2xD Flip Flop IC 7474 :  $37 \times 2 = 74$  BDT  
1x2 input OR IC : 7432 :  $30 \times 1 = 30$  BDT  
2x2 input AND IC : 7408 :  $30 \times 2 = 60$  BDT  
Total : 162 BDT

### Counter Using JK Flip Flop

Counts :

0 to 6 (Since, in combinational part 111(7) is set for Don't care)  
: 000-001-010-011-100-101-110-Repeat(000)

Current State			Next State			JK Flip Flop Outputs					
$Q_C$	$Q_B$	$Q_A$	$Q_{CN}$	$Q_{BN}$	$Q_{AN}$	$J_A$	$K_A$	$J_B$	$K_B$	$J_C$	$K_C$
0	0	0	0	0	1	1	X	0	X	0	X
0	0	1	0	1	0	X	1	1	X	0	X
0	1	0	0	1	1	1	X	X	0	0	X
0	1	1	1	0	0	X	1	X	1	1	X
1	0	0	1	0	1	1	X	0	X	X	0
1	0	1	1	1	0	X	1	1	X	X	0
1	1	0	0	0	0	0	X	X	1	X	1

### K-Maps :

$J_A$ :

$Q_C / Q_B \quad Q_A$	00	01	11	10
0	1	X	X	1
1	1	X	-	0

Eqn:  $Q_C' + Q_B'$

**K<sub>A</sub>:**

$Q_C / Q_B \ Q_A$	00	01	11	10
0	X	1	1	X
1	X	1	–	X

**Eqn: 1**

**J<sub>B</sub>:**

$Q_C / Q_B \ Q_A$	00	01	11	10
0	0	1	X	X
1	0	1	–	X

**Eqn:  $Q_A$**

**K<sub>B</sub>:**

$Q_C / Q_B \ Q_A$	00	01	11	10
0	X	X	1	0
1	X	X	–	1

**Eqn:  $Q_A + Q_C$**

**J<sub>C</sub>:**

$Q_C / Q_B \ Q_A$	00	01	11	10
0	0	0	1	0
1	X	X	–	X


**Eqn:  $Q_B \cdot Q_A$**

**K<sub>C</sub>:**

$Q_C / Q_B \ Q_A$	00	01	11	10
0	X	X	X	X
1	0	0	–	1

**Eqn:  $Q_B$**

### Circuit:

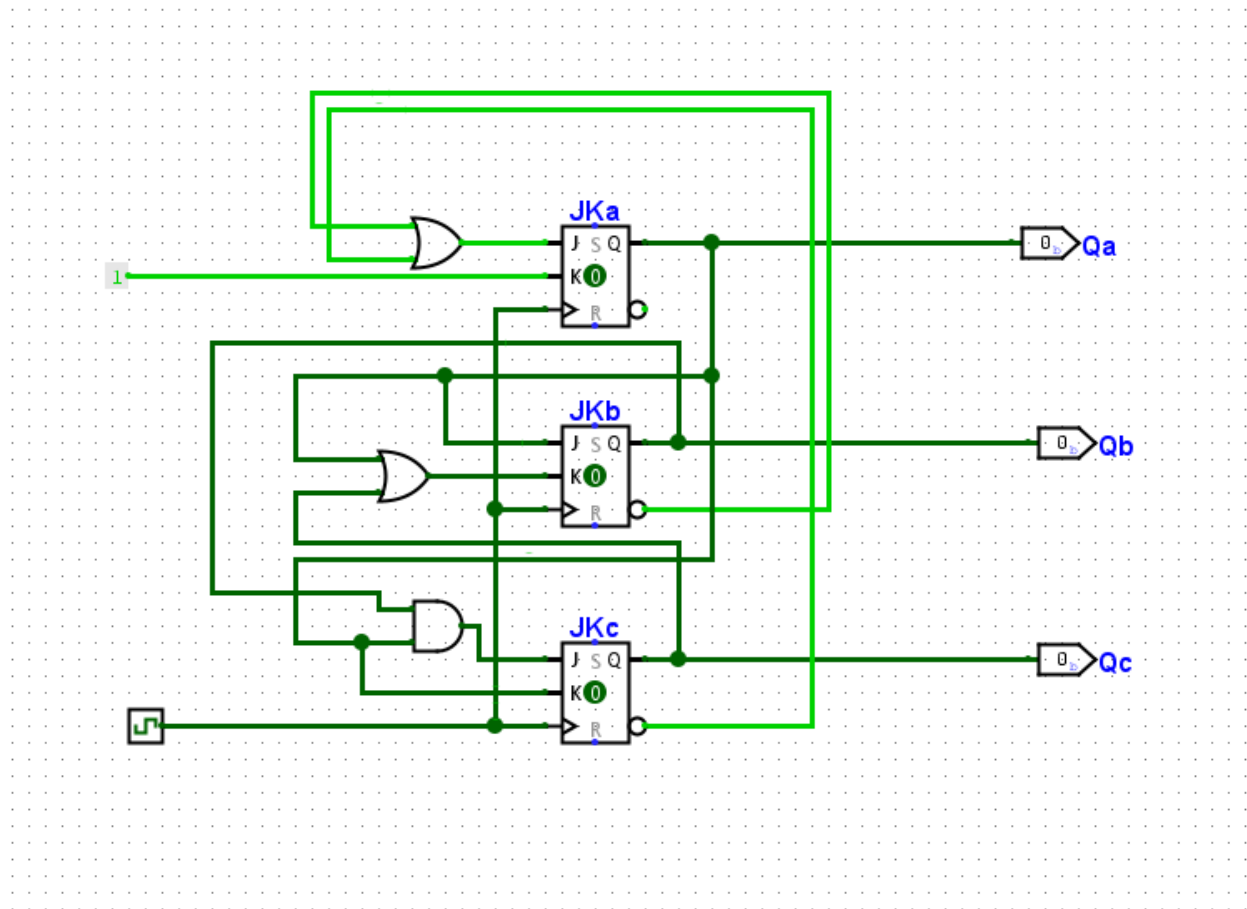

### Cost Analysis :

2xJK Flip Flop IC 7476 :  $36 \times 2 = 72$  BDT  
1x2 input OR IC : 7432 :  $30 \times 1 = 30$  BDT  
1x2 input AND IC : 7408 :  $30 \times 1 = 30$  BDT  
Total : 132 BDT